



The resistor and capacitor values are chosen with the goal that the RC time constant is about 50 ms.